

Contents

Foreword from the First Edition	xiii
Acknowledgments	xv
Introduction	xvii
About This Book	xviii
Your Electronics Lab	xxi
PART I: Playing with Electricity	1
Chapter 1: What Is Electricity?	3
Project #1: Make a Buzzer Beep	4
What Is a Buzzer?	4
How Does a Circuit Work?	5
Meet the Switch	8
Project #2: Build Your Own Secret Intruder Alarm	9
Chapter 2: Making Things Move with Electricity and Magnets	13
How Magnets Work	14
Meet the Electromagnet	15
Project #3: Create Your Own Electromagnet	17
Meet the Motor	21
Project #4: Create a Motor	22
Chapter 3: How to Generate Electricity	27
Meet the Multimeter	28
How Do Batteries Work?	29
Project #5: Turn On a Light with Lemon Power	31

PART II: Building Circuits 39

Chapter 4: Creating Light with LEDs	41
Project #6: Let's Destroy an LED	42
Meet the Resistor	44
Introducing Ohm's Law	46
Project #7: Light Up an LED Without Breaking It	51
Meet the Breadboard	53
Project #8: Your First Breadboard Circuit	56
Chapter 5: Blinking a Light	59
Meet the Capacitor	60
Project #9: Make an LED Fade Like Magic	63
Schematics	65
Meet the Relay	68
Project #10: Blink a Light!	71
Chapter 6: Let's Solder!	77
Meet the Circuit Board	78
What Is Soldering?	79
How to Solder	79
Oops! How Do I Remove a Soldered Component?	83
Project #11: Solder and Desolder Your First LED Circuit	83
Chapter 7: Controlling Things with Electricity	91
Meet the Transistor	92
Why Use a Transistor?	92
Project #12: Build a Circuit That Senses Touch	96
Resistors That Change Value	102

Measure Light with a Voltage Divider	104
Project #13: Build a Sunrise Wake-up Alarm	105
Chapter 8: Integrated Circuits: Tiny Packets of Wonder	111
Meet the Integrated Circuit	112
Meet the 555 Timer	113
Project #14: Blink a Light with an IC	116
How to Make Sound with Electricity	121
Meet the Push Button	121
Project #15: Make Your Own Electronic Musical Instrument ...	122
PART III: The Digital World	131
Chapter 9: The Basics of Digital Electronics	133
Ones and Zeros as Voltages	134
Meet the Binary Number System	134
Project #16: Convert from Binary to Decimal	136
Numbers Can Be Anything	139
Project #17: Color Guessing Game	139
Chapter 10: Circuits That Make Choices	147
What Is Logic?	148
Meet the Logic Gates	149
Negative Logic Gates	151
Logic Gates That Compare	152
How to Draw Logic Circuits	153
Using Logic Gates in Real Life	155
Project #18: A Secret Code Checker	158

Chapter 11: Circuits That Remember Information	167
Saving One Bit at a Time	168
Project #19: Light an LED with On and Off Buttons	170
A Better Memory Circuit with the D Latch	174
Memory That Changes at a Certain Time	175
Project #20: An Electronic Coin Tossers	178
 Chapter 12: Let's Make a Game!	 185
The Game You'll Build	186
Meet the Reaction Game Circuits	187
Project #21: Design an LED Reaction Game	192
Up Your Game	202
Knowledge Is Power! What Will You Build Next?.....	205
 Handy Resources	 207
Index	215