

Index

A

- American Wire Gauge (AWG), 55
- amperes (A; amps), 7, 47
- AND gate
 - converting a logic equation into a circuit diagram, 154–155
 - defined, 150
 - Light an LED with On and Off Buttons project, 174–175
 - Secret Code Checker project, 160, 162–164
- AND operator, 148–149
- anodes. *See also* LEDs
 - common anode RGB, 140–144
 - defined, 32, 43

B

- base (b), 93
- base-2 number system, 134.
 - See also* binary number system
- base-10 number system, 134
- batteries, 29–37
 - chemistry of, 30
 - compared to capacitors, 60
 - connecting in series, 30–31, 34–35
 - connecting multiple components to, 96
 - electrodes, 29
 - electrolytes, 29
 - electromagnets, 16
 - how they work, 29–31
 - lemon battery, 31–36
 - measuring voltage with multimeters, 29
 - recharging, 30
 - symbol of, 66
 - voltage, 7, 30–31

- binary number system
 - Color Guessing Game project, 139–144
 - Convert from Binary to Decimal project, 136–138
 - ones and zeros as voltages, 134
 - overview, 134–136
 - pixels, 139–144
- bits. *See also* memory circuits
 - defined, 134
 - logic equation in a secret code, 153–154
- breadboards, 53–58
 - component areas, 54–55
 - connecting divided power rails, 199
 - defined, 53
 - placing ICs on, 117–118
 - power rails, 53–54
 - wires to use with, 55–56
- Build Electronic Circuits website, 213
- buzzers
 - active, 5, 121
 - adding to LED reaction game project, 203–204
 - Build a Sunrise Wake-up Alarm project, 105–106, 108
 - Build Your Own Secret Intruder Alarm project, 9–12
 - connecting to a battery, 5–6
 - controller from code checker, 165
 - defined, 4
 - inspecting, 5
 - Make a Buzzer Beep project, 4–5
 - Make Your Own Electronic Musical Instrument project, 123–124
 - passive, 5, 121
 - piezo element, 121

C

- calculator, online, 190, 202
- capacitors, 60–65
 - capacitance, 60, 62
 - codes, 62, 209
 - compared to batteries, 60
 - defined, 60
 - farads (F), 60, 209
 - how they work, 60–61
 - LED reaction game project, 192
 - nonpolarized, 61–62
 - polarized, 61–62
 - symbol of, 66
 - types of, 61
 - values of, 62
- cathodes. *See also* LEDs
 - common cathode RGB, 140
 - defined, 32, 43
- ceramic capacitors, 209
- charges, 6–8
 - and resistance, 8
 - and voltage, 7–8
- circuit boards, 78–79.
 - See also* soldering
- Circuit Canvas website, 90, 213
- circuit diagrams, 65–67
- circuits, 5–8. *See also* digital circuits; ICs;
 - memory circuits
 - closed, 5–6, 9
 - logic circuits, 143, 153–155
 - open, 6, 9
 - schematics, 65–67
 - toggle circuit, 182–183
 - voltage divider circuit, 212
 - Your First Breadboard Circuit project, 56–58
- clock signal (CLK), 176–179
- closed circuits
 - Build Your Own Secret Intruder Alarm project, 9–12
 - creating an electromagnet, 16
 - defined, 5–6
 - and switches, 9
- collector (c), 93, 95, 98
- common anode RGB LED, 140–144
- common leg, RGB LED, 140
- common (COM) pin, 68–70

current

- charges, 6
- defined, 7
- electromagnets, 15–17
- and LEDs, 42
- multimeters, 28
- Ohm's law, 46–49
- and resistance, 8
- and voltage, 7–8

D

- datasheets
 - for integrated circuits, 113–114, 129
 - for relays, 72
- decade counter IC
 - defined, 187
 - LED reaction game project, 188–189, 192–197
- decimal numbers, 134–135, 137
- desoldering braids, 83
 - heating, 88
 - placing on the solder joint, 88
 - safety, 88
 - trimming used, 89
- D flip-flop latch
 - building ring counter with, 187–189
 - defined, 176
 - Electronic Coin Tosser project, 178–184
 - overview, 176–178
- digital circuits, 147–165
 - defined, 147
 - drawing logic circuits, 153–155
 - logic gates, 149–153, 155–156
 - making more reliable, 157
 - Secret Code Checker project, 158–165
 - true and false values, 148
 - truth table, 150–153
- digital electronics, 133–145
 - binary number system, 134–136
 - Color Guessing Game project, 139–144
 - Convert from Binary to Decimal project, 136–138
 - ones and zeros as voltages, 134
 - overview, 133–134
- D latch, 174–175
- dual in-line package (DIP) switch, 158

E

- edge triggering, 176
- electricity
 - circuits, 5–6
 - current, 6–7
 - resistance, 8
 - voltage, 7–8
- electrodes. *See also* batteries
 - defined, 29
 - Turn On a Light with Lemon Power project, 33
 - and voltage, 30
- electrolytes
 - defined, 29
 - and voltage, 30
- electromagnets
 - Create Your Own Electromagnet project, 17–20
 - defined, 14
 - how they work, 15–17
 - motors, 21
 - relays, 68
- electronics labs, xxi–xxiii
- emitter (e), 93–94, 98, 101

F

- false value, digital circuits, 148
- farads (F), 60, 209
- 555 timers
 - astable mode, 115
 - Blink a Light with an IC project, 116–121
 - defined, 113
 - Electronic Coin Tosser project, 179–182
 - LED reaction game project, 186–201
 - output frequency, 190
 - pin configuration, 114–115
 - powering, 114
 - turning the output on and off, 115
- flip-flop latch, 176.
 - See also* D flip-flop latch
- floating input, 157
- frequency
 - defined, 116
 - making sound with electricity, 121, 124–125
 - output frequency, 116

G

- ground (GND), 114
- ground rails, 54

I

- ICs (integrated circuits)
 - Blink a Light with an IC project, 116–121
 - datasheets, 113–114, 129
 - decade counter IC, 188–189, 192–197
 - defined, 111–112
 - Electronic Coin Tosser project, 181
 - 555 timers, 113
 - pin configuration, 114–115
 - powering, 114
 - Secret Code Checker project, 160
 - turning output on and off, 115
- International System of Units, 210
- inverter. *See* NOT gate

J

- joints, solder
 - bad, 82
 - defined, 79
 - desoldering, 83
 - and solder wick, 88
- jumper wires, 56

K

- kilo (k), 46

L

- LEDs (light-emitting diodes), 41–58
 - anodes and cathodes, 32, 43
 - Blink a Light! project, 71–75
 - Blink a Light with an IC project, 116–121
 - Build a Circuit That Senses Touch project, 96–102
 - controlling with transistors, 94–95
 - defined, 31–32
 - Electronic Coin Tosser project, 178–184
 - Let's Destroy an LED project, 42–44

LEDs (continued)

- Light an LED with On and Off Buttons project, 170–174
- Light Up an LED Without Breaking It project, 51–53
- Make an LED Fade Like Magic project, 63–65
- Make Your Own Electronic Musical Instrument project, 124–125
- polarized, 43
- protecting with resistors, 49–50
- RGB LED, 140–144
- on schematics, 66–67
- Secret Code Checker project, 160–161
- sensitivity of, 42
- soldering, 86
- Turn On a Light with Lemon Power project, 35
- using resistors to blink, 69–75
- Your First Breadboard Circuit project, 57
- lemon batteries, 31–36
- light-emitting diodes. *See* LEDs
- logic, defined, 148
- logic circuits. *See also* digital circuits
 - converting logic equation into circuit diagram, 154–155
 - defined, 143
 - writing logic equation for secret code, 153–154
- logic equations, 148, 153–155
- logic gates, 149–157
 - AND gate, 150
 - defined, 147, 149
 - NAND gate, 151
 - negative logic gates, 151–152
 - NOR gate, 152
 - NOT gate, 151
 - OR gate, 150
 - positive logic gates, 150–151
 - using in real life, 155–156
 - XNOR gate, 152–153
 - XOR gate, 152

M

- M (mega), 46
- mA (milliamperes), 49

magnets, 13–20

- electromagnets, 14–20
- finding magnetic objects, 15
- flexible refrigerator magnets, 15
- how they work, 14–15
- permanent, 13
- poles, 14–15, 21
- mega (M), 46
- memory circuits, 167–184
 - clock signal, 176–178
 - D latch, 174–175
 - edge triggering, 176
 - Electronic Coin Toss project, 178–184
 - flip-flop latch, 176
 - Light an LED with On and Off Buttons project, 170–174
 - negative edge-triggered, 176
 - positive edge-triggered, 176
 - SR latch, 168–170, 172, 174, 203
- microfarads (μF), 62, 209
- milliamperes (mA), 49
- motors, 21–26
 - Create a Motor project, 22–26
- multimeters
 - Build a Circuit That Senses Touch project, 101–102
 - Build a Sunrise Wake-up Alarm project, 109
 - defined, 28
 - measuring voltage of batteries, 29
 - Secret Code Checker project, 164
 - Turn On a Light with Lemon Power project, 33, 35–36
- multipliers, 45, 210

N

- NAND gate, 151
- nanofarads (nF), 62, 209
- negative edge-triggered circuit, 176
- negative logic gates, 151–152
- nonpolarized capacitors, 61–62
- NOR gate, 152
 - create an SR latch with, 168–170
 - Light an LED with On and Off Buttons project, 171–172
- normally closed (NC) pin, 68–69
- normally open (NO) pin, 68–70
- north pole (N), 14

- NOT gate
 - defined, 151
 - disarming intruder alarms, 165
 - Light an LED with On and Off Buttons project, 174
 - Secret Code Checker project, 162–163
- NPN transistor, 204

O

- Ohmify website, 213
- ohms (Ω), 44, 47
- Ohm's law, 46–50, 211
- open circuits
 - Build Your Own Secret Intruder Alarm project, 9–12
 - defined, 6
 - and switches, 9
- OR gate, 150
- oscillator circuit
 - defined, 115
 - Electronic Coin Tosser project, 181–182
 - LED reaction game project, 194
 - making sound with, 121
- output frequency, 555 timer, 190

P

- permanent magnets, 13. *See also* magnets
- photoresistors, 103–110
 - Build a Sunrise Wake-up Alarm project, 105–110
 - convert light into voltage, 104–105
 - defined, 103
 - how they work, 104
 - Make Your Own Electronic Musical Instrument project, 129
 - and voltage divider circuit, 212
- picofarads (pF), 62, 209
- piezo element
 - defined, 121
 - Make Your Own Electronic Musical Instrument project, 122–129
- pinouts, 72–73
- pixels
 - Color Guessing Game project, 139–144
 - defined, 139

- polarized capacitors, 61
- polarized LEDs, 43
- positive edge-triggered circuits, 176
- positive logic gates, 150–151
- positive rails
 - Blink a Light with an IC project, 118–120
 - defined, 54
 - Electronic Coin Tosser project, 181–182
 - LED Reaction Game project, 194–196, 198, 204
 - Light an LED with On and Off Buttons project, 173
 - Make Your Own Electronic Musical Instrument project, 125, 127–128
 - Secret Code Checker project, 159–161
- potentiometers
 - Build a Sunrise Wake-up Alarm project, 105–110
 - changing light speed, 202
 - defined, 103
 - how they work, 103
 - Make Your Own Electronic Musical Instrument, 122, 126–128
 - wiper, 103
- power rails, 53–54
- projects
 - Blink a Light!, 71–75
 - Blink a Light with an IC, 116–121
 - Build a Circuit That Senses Touch, 96–102
 - Build a Sunrise Wake-up Alarm, 105–110
 - Build Your Own Secret Intruder Alarm, 9–12
 - Color Guessing Game, 139–144
 - Convert from Binary to Decimal, 136–138
 - Create a Motor, 22–26
 - Create Your Own Electromagnet, 17–20
 - Electronic Coin Tosser, 178–184
 - LED reaction game, 192–204
 - Let's Destroy an LED, 42–44
 - Light an LED with On and Off Buttons, 170–174
 - Light Up an LED Without Breaking It, 51–53
 - Make a Buzzer Beep, 4–5

projects (continued)

- Make an LED Fade Like Magic, 63–65
 - Make Your Own Electronic Musical Instrument, 122–129
 - Secret Code Checker, 158–165
 - Solder and Desolder Your First LED Circuit, 83–89
 - Turn On a Light with Lemon Power, 31–36
 - Your First Breadboard Circuit, 56–58
- pull-down resistors, 157, 171
- push buttons
- Electronic Coin Tosser project, 180–181
 - LED reaction game project, 191, 193
 - Make Your Own Electronic Musical Instrument project, 122–128
 - overview, 121–122
 - pin configuration, 122

R

red-green-blue (RGB) LED

- Color Guessing Game project, 139–144
- common anode RGB, 140–144
- common cathode RGB, 140
- common leg, 140
- overview, 140–141

relays, 68–75

- Blink a Light! project, 71–75
- coils, 69
- datasheets for, 72
- defined, 68
- making an intruder alarm more effective, 75
- pinouts, 72
- pins, 69, 72–73
- using to blink a light, 69–70

resistance

- determining resistance value, 50
- multimeters, 28
- Ohm's law, 46–49, 211
- resistor color codes, 45
- slowing charges down, 8

resistors, 44–46

- color codes, 45–46, 51–52
- defined, 44
- determining resistance value, 45–46, 51–52
- disarming intruder alarms, 165

- finding, 42
- multiplier, 45
- ohms, 44
- Ohm's law, 48–49
- photoresistors, 103–110
- potentiometers, 103, 105–110
- protecting LEDs with, 49–50
- pull-down resistors, 157, 171
- resistor color codes, 208
- on schematics, 66–67
- soldering, 86
- tolerance, 45–46
- variable resistance, 102–110
- voltage divider circuit, 212

resources, 207–213

- capacitor codes, 209
- Ohm's law, 211
- online electronics shops, 212–213
- online tutorials and project ideas, 213
- resistor color codes, 208
- standard prefixes, 210
- voltage divider circuit, 212

RGB (red-green-blue) LED

- Color Guessing Game project, 139–144
 - common anode RGB, 140–144
 - common cathode RGB, 140
 - common leg, 140
 - overview, 140–141
- ring counter, 187–188

S

- safety, xxiii, 20, 22, 31, 80, 88, 101
- schematics, 65–67

sensors

- Build a Circuit That Senses Touch project, 96–102
- defined, 95–96
- single-strand wires, 55
- soldering, 78–90
 - adding solder, 81
 - bad joints, 82
- circuit boards, 78–79
- defined, 79
- heating the pin and pad, 81
- inserting the components, 81
- irons
 - cleaning the tip, 81, 86
 - defined, 79

- heating, 80, 86
 - removing, 82
- joints, 79, 82, 83, 88
- removing soldered components, 83
- safety, 80
- Solder and Desolder Your First LED
 - Circuit project, 83–89
 - tools for, 79
- solder wicks
 - desoldering, 83
 - heating, 88
 - placing on solder joint, 88
 - safety, 88
 - trimming used, 89
- south pole (S), 14
- SR latch memory circuit
 - LED reaction game project, 202–203
 - Light an LED with On and Off Buttons
 - project, 172, 174
 - overview, 168–170
- switches, 8–12
 - Blink a Light! project, 73–74
 - Build Your Own Secret Intruder Alarm
 - project, 9–12
 - defined, 8
 - DIP switch, 158
 - relays, 68
 - Secret Code Checker project, 159, 163
- synthesizers, 122

T

- tantalum capacitors, 209
- toggle circuit, 182–183
- tolerance, 45–46
- transistors, 92–102
 - base, 93
 - Build a Circuit That Senses Touch
 - project, 96–102
 - Build a Sunrise Wake-up Alarm
 - project, 105–110

- collector, 93, 95, 98
- controlling LEDs with, 94–95
- defined, 92
- disarming intruder alarms, 165
- emitter, 93
- how they work, 93–94
- LED reaction game project, 204
- leg placement, 98–99
- and logic gates, 156
- reasons for using, 92
- Secret Code Checker project, 161
- true value, digital circuits, 148
- truth table, 150–153
- tutorials, online, 205

V

- variable resistors, 102–104
 - photoresistors, 103–110
 - potentiometers, 103, 105–110
- V_{CC} pins, 114
- voltage, 174
 - of batteries, 29–31
 - clock signal, 176–178
 - multimeters, 28
 - Ohm's law, 46–49
 - ones and zeros as, 134
 - pushing charges, 7–8
- voltage dividers
 - Build a Sunrise Wake-up Alarm
 - project, 105–109
 - defined, 212
 - how they work, 104
- volts (V), 7, 47

X

- XNOR gate, 152–153
- XOR gate, 152